 


# An Ultra-Broadband Power Amplifier Design

Chung-Ho Chai

Advisor : Prof. Yu-Jiu Wang






Department of Electronics Engineering  
National Chiao-Tung University  
Hsin-Chu, Taiwan

# Outline

- Motivation and Architecture
- Amplifier Design and Transistor's Modeling
- Passive Circuit Design and Analysis
- Simulation and Measurement Results
- Debugging Discussion


   
# Motivation- Concurrent Dual-band, Dual-mode TRX Rainfall Detection




RF signal attenuation
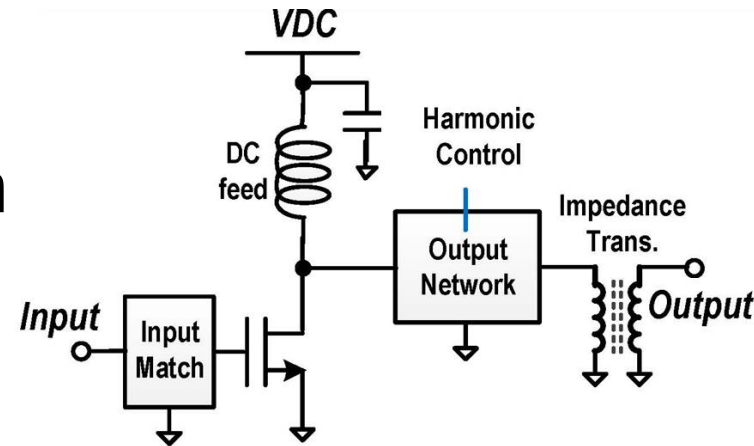
# Block Diagram of Power Amplifier

- Output Network


- Impedance Transformation
- Power Combining
- Harmonic Control



- (1) Filtering: Only 1<sup>st</sup> harmonic tone passed to the 50Ω load.
- (2) To shape **transistor's output** I/V waveform provides necessarily impedance at different harmonics for e.g. class F, class J.
 
# Cascode Topology

- Thick Gate Oxide Device
  - higher breakdown voltage
  - lower process speed
- Common Gate Amplifier
  - improve twice PA's max. output voltage swing
  - $V_{gs}$  is limited by M1



# CG PA Size Choosing, Bias Conditions

- PA Design Flow:

1. M1's breakdown  $V_{DS} = 1.2V, V_{GS,GD} = 1.5V$

$$V_{G2} = V_{D1}(\text{max}) + V_{th2} = 1.5 + 0.6 = 2.1V$$



M2's breakdown  $V_{DS} = 2.7V, V_{GS,GD} = 4.5V$

$$V_{DD} = V_{D1}(\text{DC}) + V_{knee2} + V_{DS2}(\text{swing}) = 1 + 0.5 + 1 = 2.5V$$

  2. With limited  $V_{D1}$  headroom and  $V_{DS2}(\text{max})$ , M2's size corresponds to target output power.


- M2 Size  $\propto$  current magnitude  $\propto$  output power  $\propto \frac{1}{R_{load}}$
- the same  $V_{knee}$  with different sizes

- Drain efficiency depends on input waveform



 
# CS Driver Size Choosing, Bias Conditions

- $Z_{load} = 1/G_{m2}$  paralleled with parasitic caps on inter-node
- $V_{D1_{max}} = 1.5V$  based on breakdown criteria
- $I_{1_{max}} = I_{2_{max}} \times \frac{\sqrt{(G_{m2}^2 + (\omega_o C_p)^2)}}{G_{m2}}$ ,  $C_p$  is parasitic cap. at D1 node



 - $V_{G1_{min}} = V_{D1_{max}} - V_{DG}(\text{breakdown})$
- $V_{G1_{max}} = V_{GS1}(\text{breakdown})$
- $V_{G1}(\text{bias}) = (V_{G1_{max}} + V_{G1_{min}})/2 = 0.8V$
- M1 size: when gate voltage swing “touch” the triode region




# Oscillation Conditions

- Barkhausen Criterion: loop gain  $|\beta H(\omega)| \geq 1$  and  $\angle \beta H(\omega) = 180^\circ$

$$\beta H(\omega) = \frac{(sC_{ds} + \frac{1}{r_o})(sL + R_L)(1 - s\frac{C_{ds}}{G_M})}{(1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}})(1 + \frac{s}{\omega_{p3}})}$$
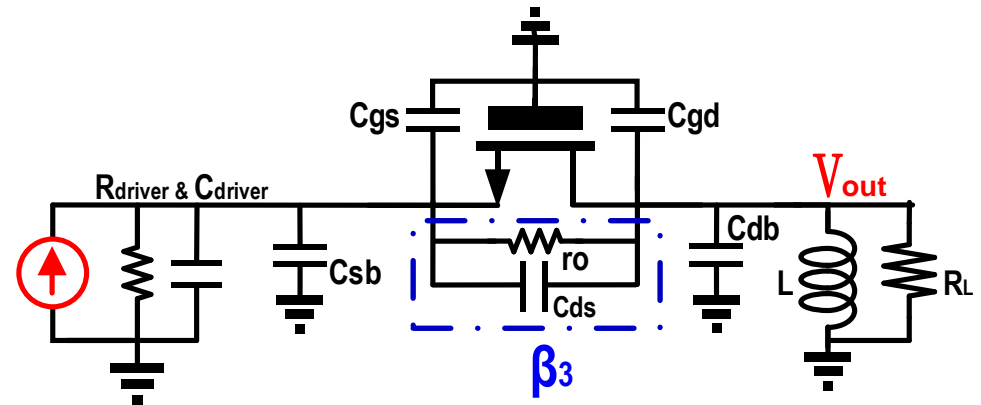
$$\omega_{p1}, \omega_{p2}, \omega_{p3} \text{ equals to } \frac{1}{R_L C_{out}}, \frac{1}{R_{in} C_{in}}, \frac{R_L}{L}$$




- Oscillation Conditions:

If  $\omega_{p1} \gg \omega_{z2}$  and  $|\beta H(\omega)| > 1$  b.t.  $\omega_{z2}$  to  $\omega_{p1}$



# Simplified Chip Block Diagram

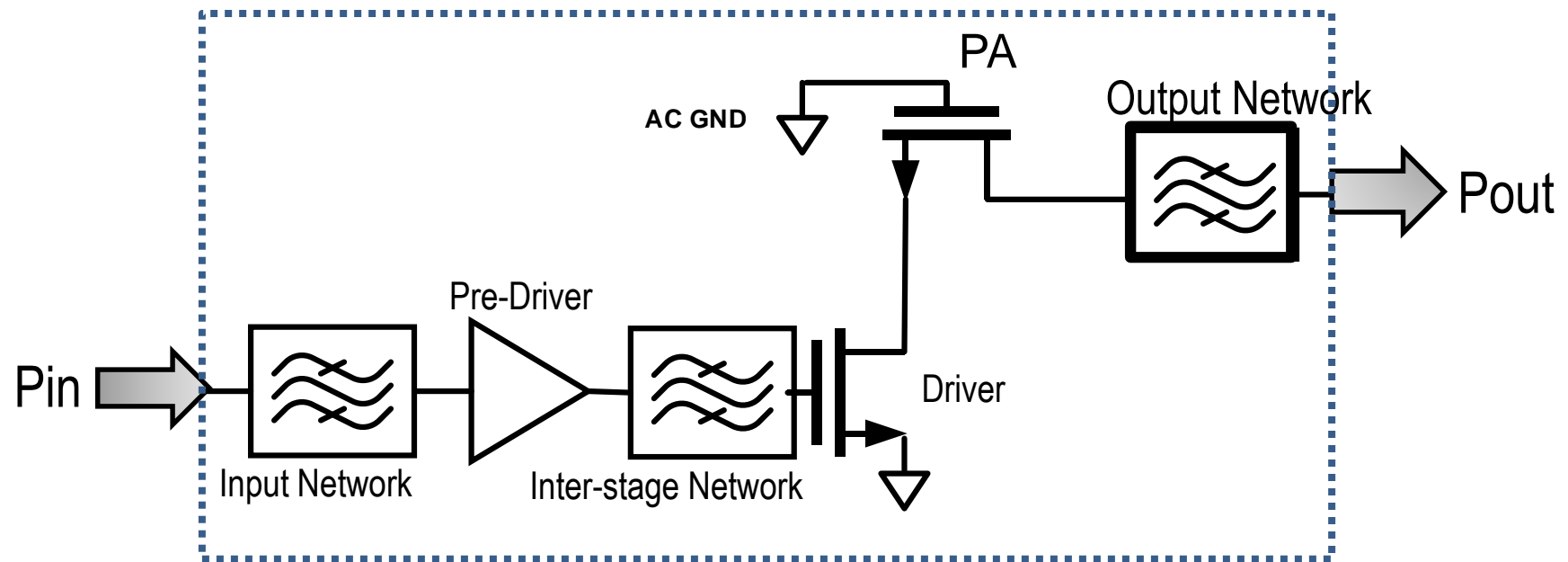


# PA Specifications

- $P_{SAT}$  : MAX power whole PA could deliver = PA's maximum drain power \* efficiency of output network

- $$PAE = \frac{P_{out} - P_{in}}{P_{DC}} = \frac{Eff_{output} G_{PA} G_{driver} P_{in} - P_{in}}{P_{DCPA} + P_{DCdriver}} \cong \frac{Eff_{output} * G_{PA}}{\frac{G_{PA}}{\eta_{pa}} + \frac{1}{\eta_{driver}}}$$

where  $\eta$  = transistor's drain efficiency =  $\frac{P_{RFOUT}}{P_{DC}}$

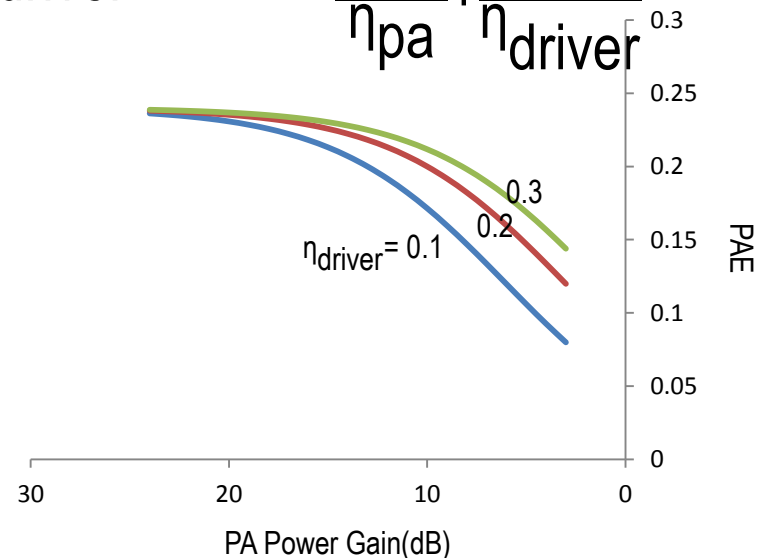and assume  $Eff_{output} G_{PA} G_{driver} \gg 1$




交通大學

National Chiao Tung University


# Power Transistor Design

- Determine how to connect multi-finger transistors in parallel
  - layout placement and metal's reliability to DC/AC current
  - reduce parasitic R,C related to output power/bandwidth performances
- Modeling, optimization
 
# Single Transistor Layout Structure Design for Common Gate


 
# Parallel Combining of multi-finger Transistors



# PA - Common Gate Amplifier


- $\beta = \frac{1}{Z_{C_{DS}}} = j\omega C_{DS}$ ,  $H_{close} = \frac{H_{open}}{1 + H_{open}\beta}$  (Transimpedance Gain)

- $R_g$ : decrease the equivalent  $G_m$  when freq. increase

$$V_{GS} = \frac{Z_{C_{gs}}}{R_g + Z_{C_{gs}}} V_s = \frac{1}{j\omega R_g C_{gs} + 1} V_s$$


$R_g$ : Insert Gate to Body bypass using MOS Cap. between two multi-finger transistors (the same finger # with transistors beside)

$$R_{g_{new}} = R_g // Z_{bypass}$$

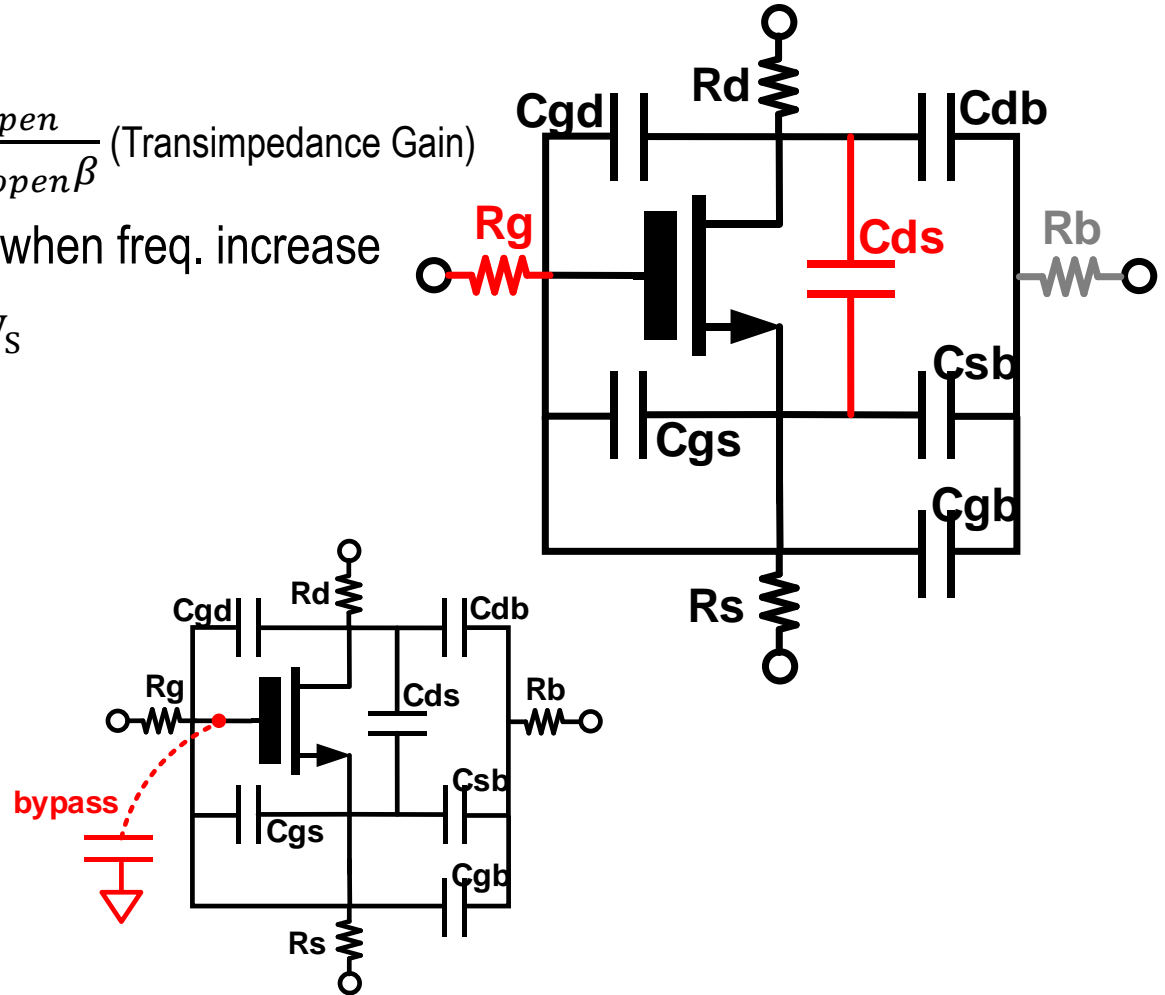

# Modeling of Layout Parasitic

- effective resistance

 


(e.g.) If  $I_1 = I_2 = \dots = I_n = I$ , and  $R_1 = R_2 = \dots = R_N = R$


$$I^2 \times R + (2I)^2 \times R + \dots + (NI)^2 \times R = (NI)^2 \times R_{eff}, \quad R_{eff} = \frac{(N+1) \times (2N+1)}{6N} R \cong \frac{1}{3} NR \quad (\text{if } N \text{ is large})$$

- to model parasitic Caps. by interpolation of PEX results

 
# Common Gate Power Transistor Optimization



(a)  $R_g$  (total)

 


(b)  $R_s$

 

(c)  $R_d$


 
- (1) fix total  $W$ , minimize  $R_x(w, nr)$
- (2) metal reliability criteria with min.  $C_{ds}$ ,  $nr \leq \alpha^*(160/w)$



(e.g.) Total Width=3000  
 $w=3.3\mu\text{m}$ ,  $nr=90$ ,  $M=10$



 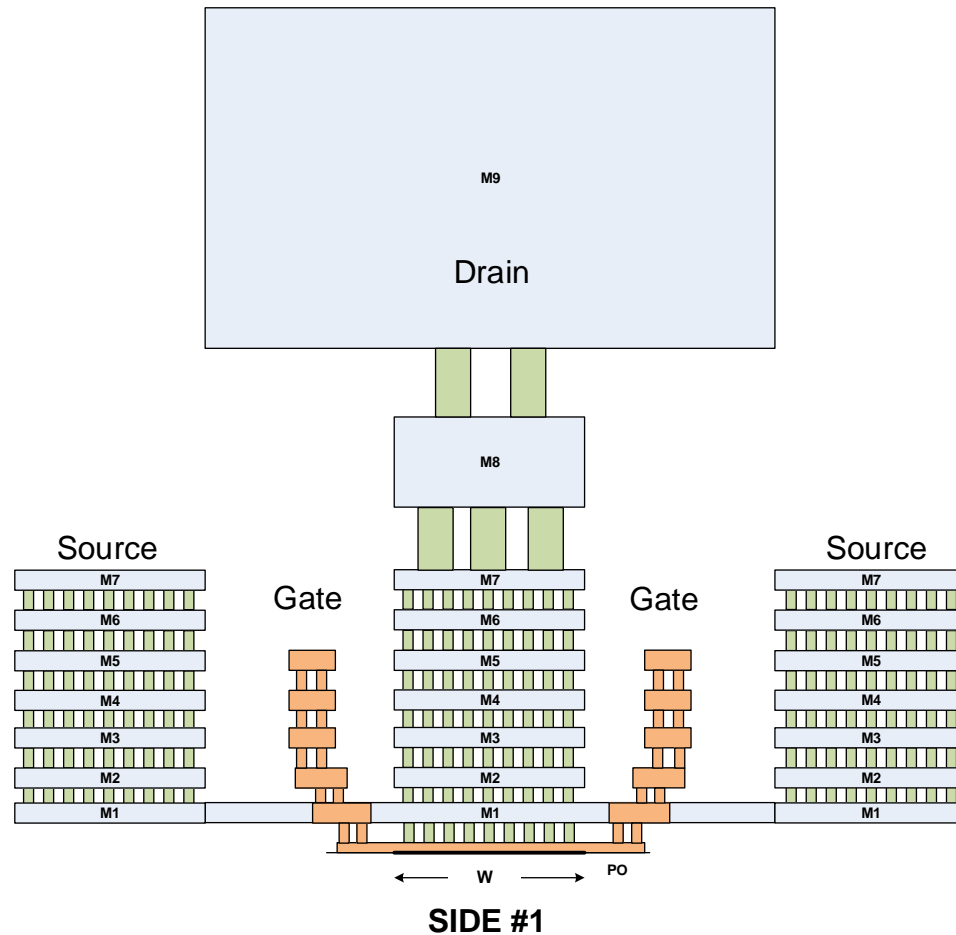
# Single Transistor Layout Structure Design for Common Source


 
# Broadband Optimum Load & Passive Output Network

- $\frac{Q_{\text{load}}}{\omega_0} = \frac{1}{R_{\text{load}} C_{\text{out}}} \propto \text{3dB Bandwidth}$



$$(1) \tau_{\text{network}} = R_L C_L \geq R_{\text{opt}} C_{\text{out}} = 2 \frac{V_{\text{swing}}}{V_{\text{in}}} \times \frac{C_{\text{out}}}{G_m}$$

$$V_{\text{swing}} \leq \frac{1}{2} \tau_{\text{network}} \times \frac{G_m}{C_{\text{out}}} \times V_{\text{in}}$$

(2) impedance transformation ratio

(3) network's passive efficiency

$$R \cong \frac{\max V_{\text{swing}}}{I_{\text{swing}}}$$



$$C \cong -(C_{DG} + C_{DB} + C_{DS})$$



交通大学

National Chiao Tung University
  
# To Define Two-Port Band-pass LC-Ladder Network



- Bode-Fano limit:  $\int_0^\infty \ln \frac{1}{|\Gamma(j\omega)|} d\omega \leq \pi \left( \frac{1}{R_{\text{opt}} C_{\text{out}}} \right)$
- Passive Ladder:  $|S_{21}(s)|^2 = H(\omega^2) = \frac{1-C}{1+C \cdot \frac{A_N s^{2N} + A_{N-1} s^{2(N-1)} + \dots + A_1 s^2 + A_0}{s^{2M}}} = \frac{1-C}{1+C \cdot F}$
- Chebyshev Filter : find  $F \in [-1, 1]$  with  $\omega \in [\omega_L, \omega_H]$
- Relations among ripple, N to BW, impedance transformation ratio


# Darlington's Insertion-loss Method

## • General Procedures:

1. Find out  $|S_{21}(s)|^2$  as a function of  $\omega^2$ .
2. Determine  $|S_{11}(s)|^2 = 1 - |S_{21}(s)|^2$ .
3. Determine all possible  $S_{11}$  from  $|S_{11}|^2$ .
4. Determine  $Z_{11} = \frac{1+S_{11}}{1-S_{11}}$  from each  $S_{11}$ .
5. Determine all possible realizations of  $Z_{11}$  and choose the best one.


(e.g.)  $Z_{11} = sL + Z'_{11}$ ?  $Z'_{11}$  is reduced-order, and has no pole at  $\omega = \infty$ .

 $Z_{11} = \frac{1}{sC} + Z'_{11}$ ?  $Z'_{11}$  is reduced-order, and has no pole at  $\omega = 0$ .






# Node Parasitic Cap. Compensation

- Norton's Transformation

 

$$K = \frac{Z_p}{Z_p + Z_s}$$

- (e.g.)

   



# Limitation of Broadband Load Tracking

- $|S_{11}|^2 + |S_{21}|^2 + \text{power loss(ratio)} = 1$ , when loss is large, load tracking failed.
  - How to define wideband flat  $Z_{\text{out}}$  Synthesis ?
  - How to formulate passive efficiency, impedance transform ratio and bandwidth?


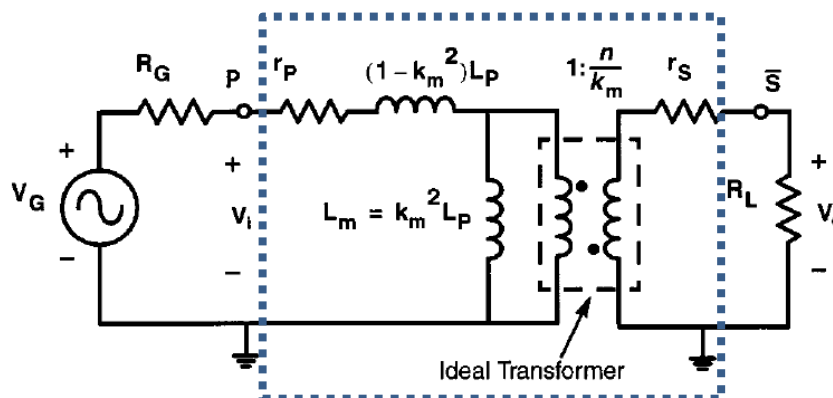 
# Output Network

- Impedance transformation ratio  $\eta_{\text{diff}} = 4\eta_{\text{com}}$
- Insert transformer to network




- $\frac{k_m^2 L_p}{(1 - k_m^2) L_p}$  is positively correlated with network's bandwidth  
 $\rightarrow$  network BW  $\uparrow$  required transformer's  $k_m \uparrow$
- Transformer's passive efficiency




 
# Pre-Driver & Inter-Stage Network

- Pre-driver stage operates in Class-A mode to improve gain and linearity.
  - cascode amplifier with  $\left(\frac{W}{L}\right)_{nch} = \frac{250 \mu m}{0.06 \mu m}$  and  $\left(\frac{W}{L}\right)_{nch25} = \frac{530 \mu m}{0.28 \mu m}$
  - Ratio of driver's max. input voltage and pre-driver's max output voltage
- ➔ impedance transformation ratio of interstage network






# Full-Chip Schematics & Layout

 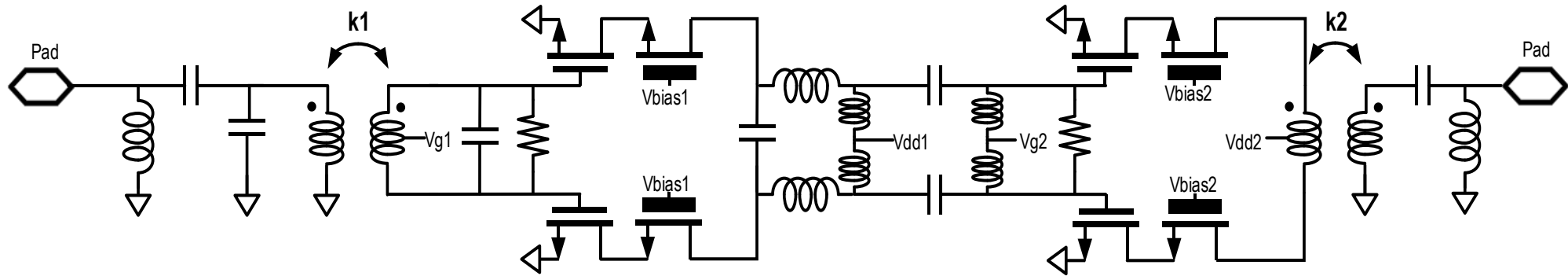


# Chip Micrographs

 


Chip Area:	$1614 \times 675 \text{ } \mu\text{m}^2$
DC Power Consumption:	$2.5\text{V} \times 960 \text{ mA}$


 
# Full Pre-Simulation (red line) vs. Measurement (blue line)




 
# Full Post-Simulation (red line) vs. Measurement (blue line)



交通大學

National Chiao Tung University

# Output Network

  

freq (5.800GHz to 24.00GHz)



交通大學

National Chiao Tung University


# Output Network – Transformer modeling errors

PORT1: Differential Input PORT

PORT2: Output PORT


Red line: EM S2P

Blue line: Model

 


freq (100.0MHz to 30.00GHz)

$S(1,1)$

 

freq (100.0MHz to 30.00GHz)

$S(2,2)$

 

freq (100.0MHz to 30.00GHz)

$S(2,1)$




交通大學


National Chiao Tung University

# Output Network


## Output Power

 



## Passive Efficiency

 

## Diff. to single S(2,1)

 

## Input Impedance

  


500mA RF current & 2pF device output cap. assumed  
Network is designed from 5Ω to 50Ω



交通大學

National Chiao Tung University

# Interstage Network

 


- $L1=55\text{pH}$ , which is sensitive to parasitic TLine1
- $C1=3.98\text{pF}$ , which has visible parasitic L effect, but not model in network synthesis Model
- CS PA driver input feed lines, parasitic TLine2, change the frequency response of network






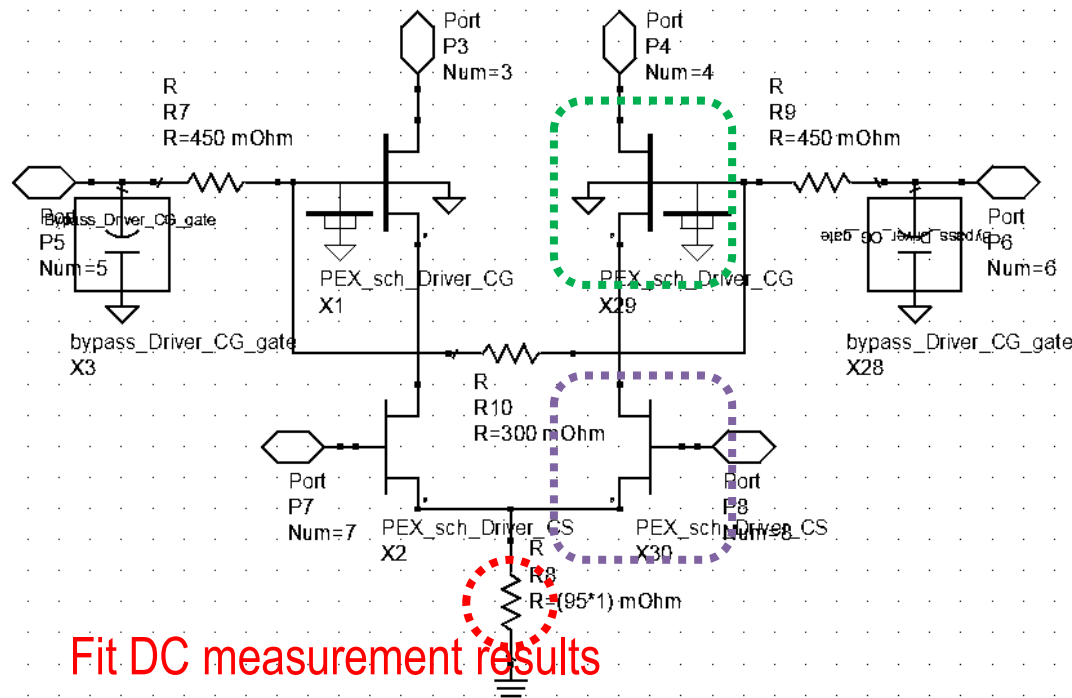
# Fit Transistor parasitic RC by PEX results




## Fit DC measurement results

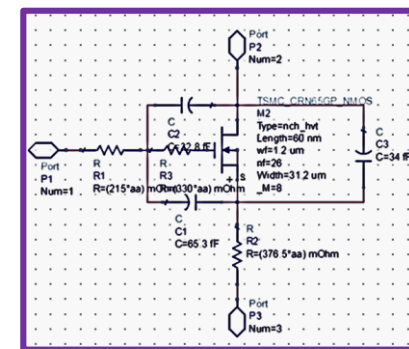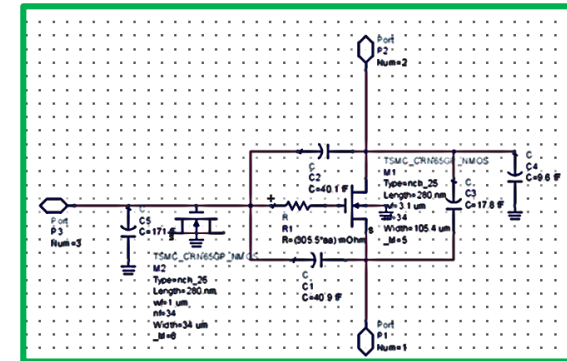

 
# Input Network

- To affect input matching accuracy (XFM model error)
- Tiny effects to S21


 
# Power Transistor Model Accuracy

- De-embed measurement S-parameter with output network EM results
  - Transfer [S] to [T]
  - $[T]_{\text{de-embed}} = [T]_{\text{chip}} * [T]_{\text{network}}^{-1}$
  - Transfer  $[T]_{\text{de-embed}}$  back to [S]
- To model “skin effect” of R
- To model L from EM



# My Suggestion to This Work's Future

- Target smaller power& use nch to replace nch25
- Thank you.



# Appendix




交通大學

National Chiao Tung University

7/16/2014
 
# Ultra-Broadband Considerations


- In-Band Harmonics Problem in Ultra-Broadband Scales
    - At relative low frequency, 2<sup>nd</sup> and 3<sup>rd</sup> harmonic tones would be in-band.
- It CANNOT be filtered!!!



- Broadband push-pull output network cancels 2<sup>nd</sup> harmonic
- Broadband poly-phase combining network cancels both 2<sup>nd</sup> and 3<sup>rd</sup> harmonics



# Gate Oxide Breakdown

 

- Catastrophic damage caused by excessive voltage across gate oxide
- Probabilistic: lifetime decreases with voltage and device area
- Determined by oxide thickness and quality

1.0V Core Device  
(W/L=1.4mm/60nm)

$V_{GD} \text{ max}=1.5V$

2.5V I/O Device  
(W/L=3 mm/280nm)

$V_{GD} \text{ max}=4.5V$

Must keep max  $V_{GD}$ ,  $V_{GS}$  within limit for gate oxide breakdown.




交通大學

National Chiao Tung University
 
# $V_{DS}$ Breakdown Mechanism

- Hot Carrier Injection Effect
  - gradual device performance degradation over a period of time
  - necessary to have high drain-source voltage,  $V_{DS}$ , and substantial drain current at the same time
  - Max  $V_{DS}$  of 1.0V 65nm NMOS: 1.18V  
Max  $V_{DS}$  of 2.5V I/O NMOS: 2.70V



- Punch-Through ( $V_{DS}$ )  
65nm NMOS=3.0V



# Precise Model of Gate Resistor Network

R<sub>g</sub> network:

Differential Mode:

symmetric line of layout is A.C ground


Common Mode:

symmetric line of layout is open

$$R_g = 4(R_g // R_{g'}), \quad R_{g'} = \frac{R_g}{3}$$


$$Z_g(\text{diff}) = R_g // \frac{R_g}{3} // Z_{\text{bypass}} + R_{\text{poly}}$$
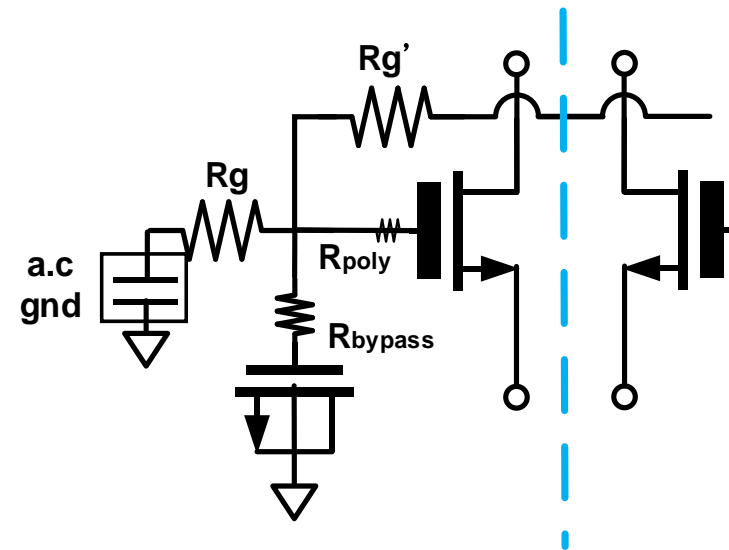
$$Z_g(\text{com}) = R_g // Z_{\text{bypass}} + R_{\text{poly}}$$



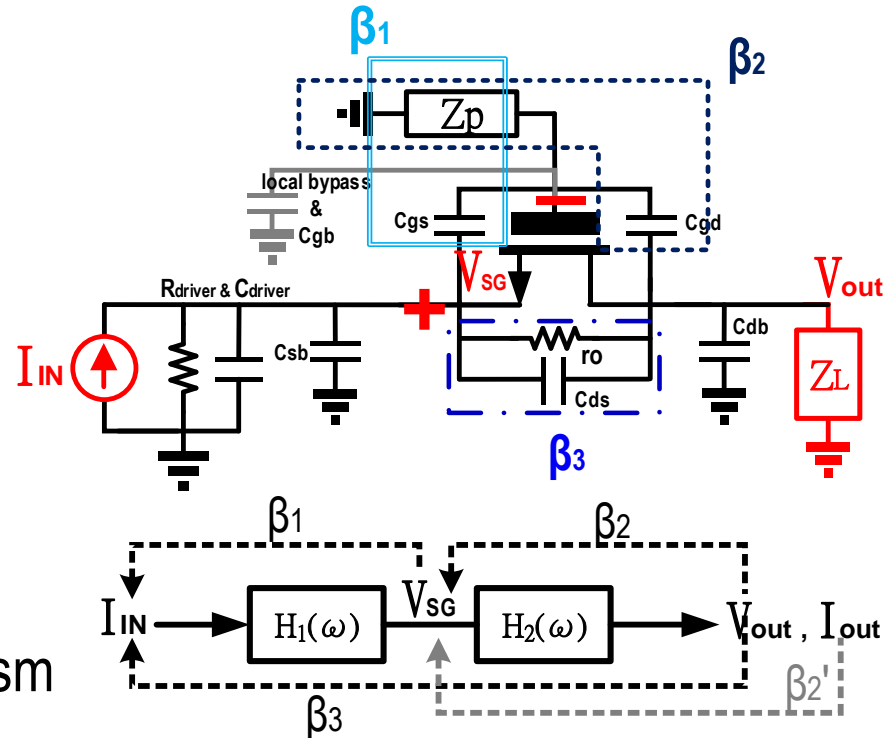
# Oscillation Conditions in details

- Feedforward:  $s_z = +\frac{G_M}{C_{DS}}$ ,  $f_z$  is larger than 100GHz in 0.28  $\mu\text{m}$  I/O device.
- Positive Feedback:
  - $\beta_1, \beta_2$ : series-shunt feedback
  - $\beta_3$ : shunt-shunt feedback
- Insert Local Bypass Caps:
  - $Z_{p_{\text{new}}} = Z_p // Z_{\text{bypass}}$
  - kill  $\beta_1, \beta_2$  feedback mechanism





P.S.  $\beta_2'$ : series-series feedback, inductive coupling b.t.  $Z_L$  &  $Z_p$

# Effective Negative Port Resistance

 

- If  $Z_1 = \frac{1}{j\omega C_{DS}}$ ,  $Z_2 = R + j\omega L$ , we get  $j\omega L \parallel \frac{1}{G_m(1 - \omega^2 C_{DS} L)}$  at high frequency if  $R$  is small.
  - a) narrow band short-stub matching
  - b) XFM common-mode inductor

Example:

  


交通大學

National Chiao Tung University

# “ $|S_{11}|^2 \rightarrow S_{11}$ ” Enumerations


- $|S_{11}|^2 = S_{11}(s)S_{11}(-s) = \frac{\prod_m (r_{z,m}^2 - s^2) \prod_n (r_{z,n}^2 + s^2)^2 \prod_o (s + r_{z,o} + jx_{z,o})(s + r_{z,o} - jx_{z,o})(s - r_{z,o} + jx_{z,o})(s - r_{z,o} - jx_{z,o})}{\prod_i (r_{p,i}^2 - s^2) \prod_j (r_{p,j}^2 + s^2)^2 \prod_k (s + r_{p,k} + jx_{p,k})(s + r_{p,k} - jx_{p,k})(s - r_{p,k} + jx_{p,k})(s - r_{p,k} - jx_{p,k})}$

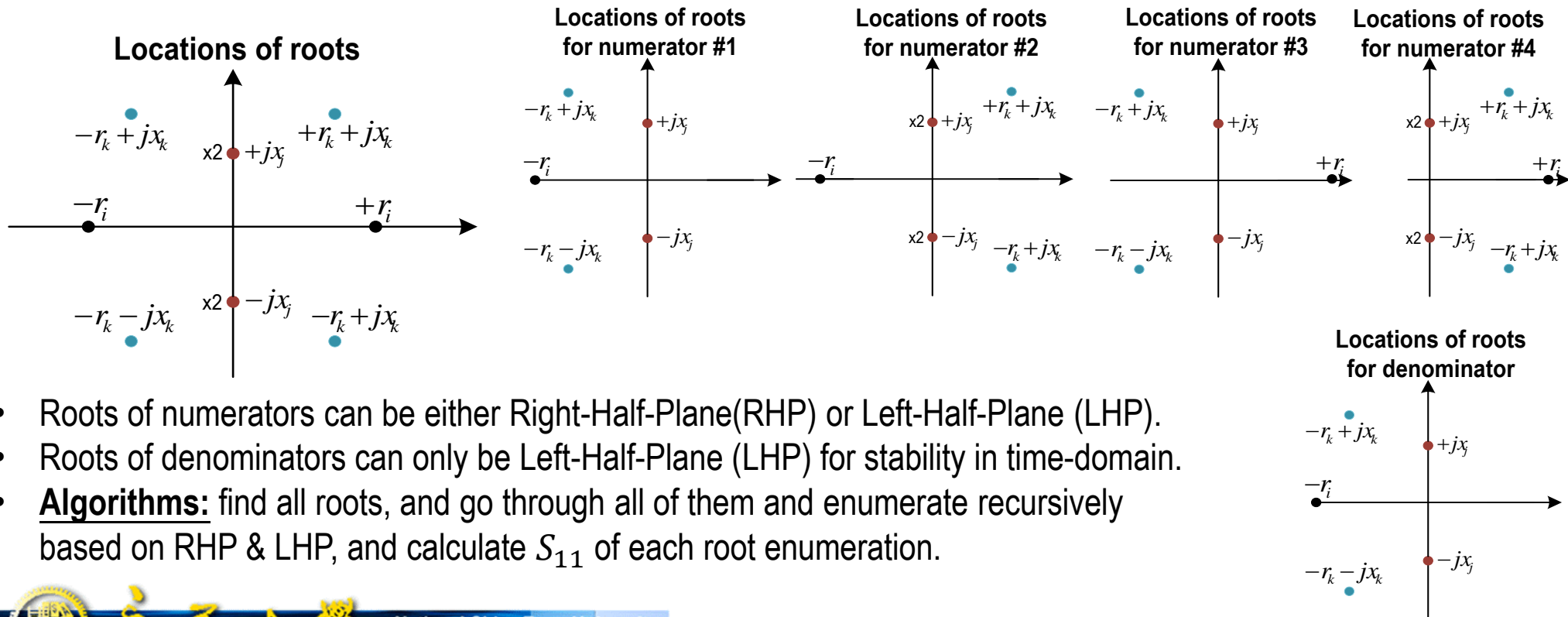

- Roots of numerators can be either Right-Half-Plane(RHP) or Left-Half-Plane (LHP).
- Roots of denominators can only be Left-Half-Plane (LHP) for stability in time-domain.
- Algorithms:** find all roots, and go through all of them and enumerate recursively based on RHP & LHP, and calculate  $S_{11}$  of each root enumeration.
 
# Efforts to Improve Transformer's Model

LAYOUT: more tuning degree of freedom to fit model



MODEL: parasitic estimation improvement (R,C)




交通大學


National Chiao Tung University

# Output Network - Imbalanced Problem

- Transformer unbalanced problems

 
 
$$i_{s1} = i_{s2} + i_{gnd2}$$
$$i_{p1} \neq i_{p2}$$





Ref: "Two-Way Current-Combining W-Band Power Amplifier in 65-nm CMOS", Qun Jane Gu, Zhiwei Xu, and Mau-Chung Frank Chang




交通大學

National Chiao Tung University

# Output Network - Imbalanced Problem

 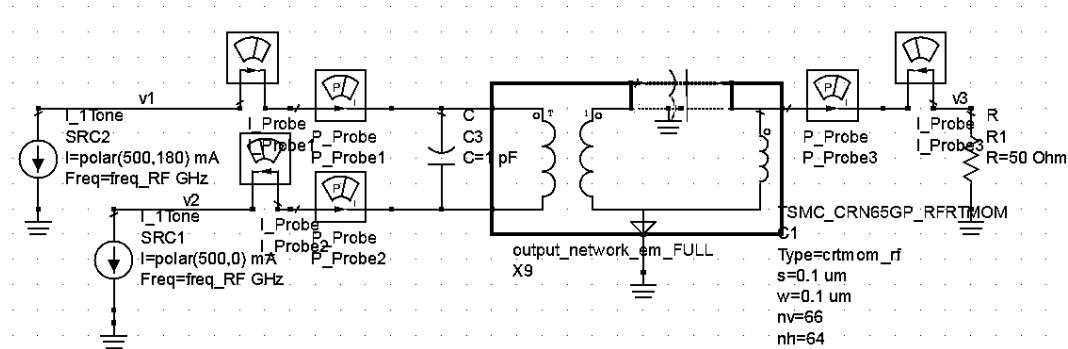

 If we put center-tap bypass and effective PA “C<sub>out</sub>” to GND



# Class J - Class AB Using a Capacitive Harmonic Termination

- Fundamental Impedance: loadline impedance  $R_L$   
Second harmonic:  $X_{out}/2$
- Trade-off: Larger Peak Voltage at Output Node

